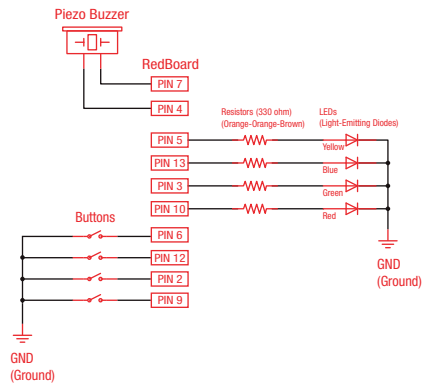


CIRCUIT #16

16

Simon Says

Now that we've learned all the basics behind the components in the SIK, let's put them together and have some fun. This circuit will show you how to create your own Simon Says game. Using some LEDs, some buttons, a buzzer and some resistors, you can create this and other exciting games with your SIK.




PARTS:

330Ω
Resistor



x 4

LED

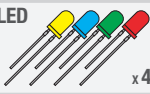

x 4

Push Button



x 4

Piezo Element





x 1

Wire





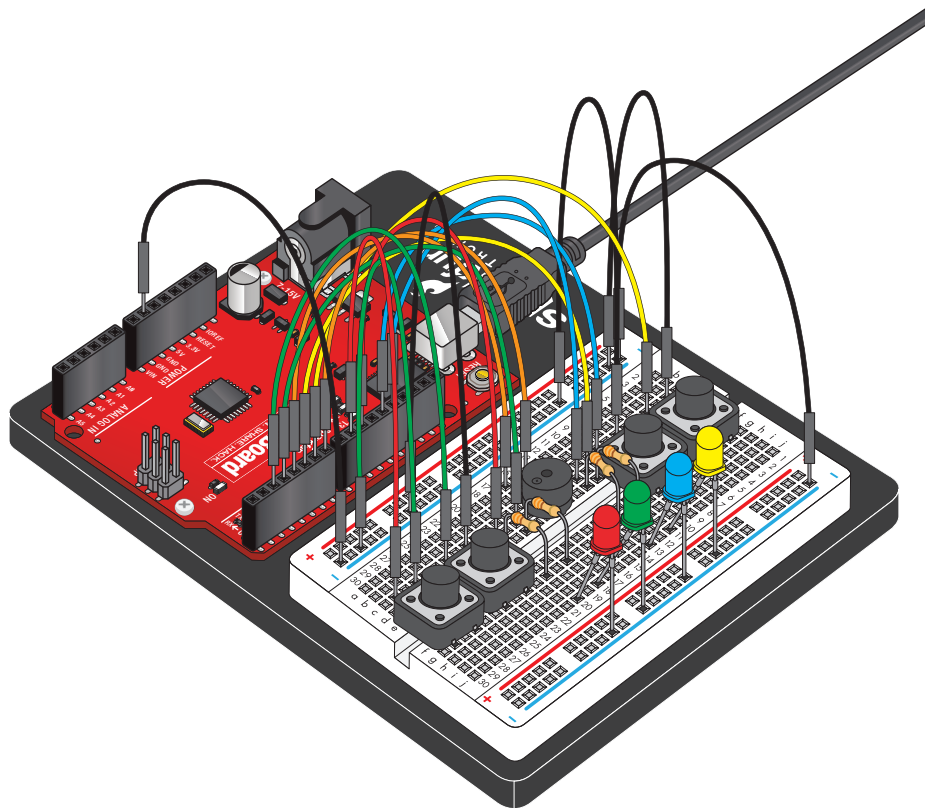

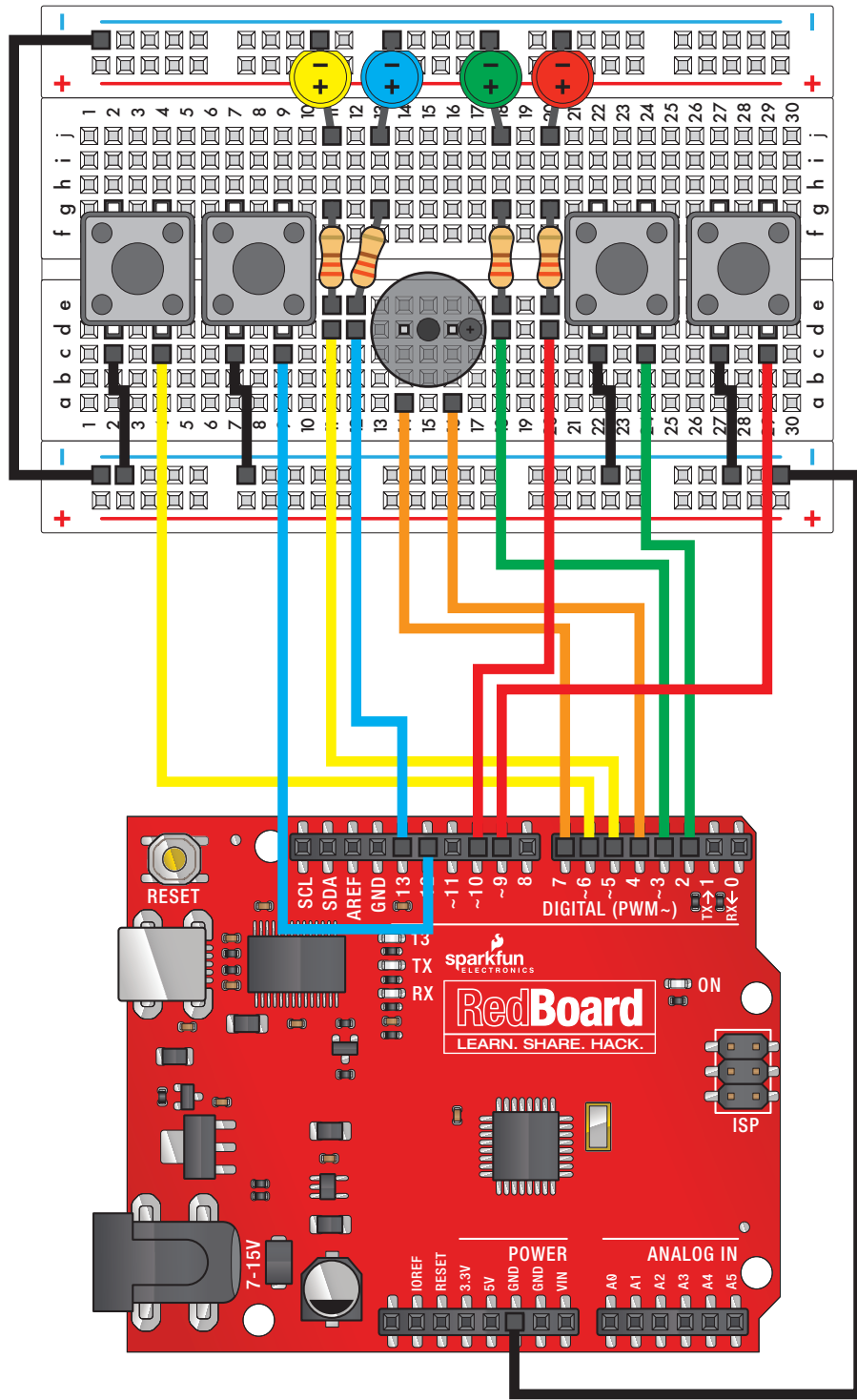














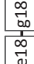
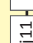



















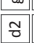











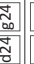









x 16





Circuit 16: Simon Says

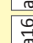 Component:	Image Reference:			Component:	Image Reference:	
330Ω Resistor				Jumper Wire		
330Ω Resistor				Jumper Wire		
330Ω Resistor				Jumper Wire		
330Ω Resistor				Jumper Wire		
				Jumper Wire		
LED (5mm)				Jumper Wire		
LED (5mm)				Jumper Wire		
LED (5mm)				Jumper Wire		
LED (5mm)				Jumper Wire		
				Jumper Wire		
Push Button				Jumper Wire		
Push Button				Jumper Wire		
Push Button				Jumper Wire		
Push Button				Jumper Wire		
Piezo Element				Jumper Wire		

16

Arduino Code:



Open Arduino IDE // File > Examples > SIK Guide > **Circuit #16**

Code to Note:



#define



The `#define` statement is used to create constants in your code. Constants are variables that will likely only have one value during the lifespan of your code. Thus, you can assign constants a value, and then use them throughout your code wherever you need them. Then, if you need to change that value, you only have to change one line instead of going through all the code to find every instance of that variable.


byte



Bytes are another variable type. In the world of computing, a byte is a chunk of space that contains 8 bits, and a bit is a single binary value. Binary is another way of counting and uses only 1's and 0's. So a byte can hold all 1's: 11111111, all 0's: 00000000, or a combination of the two: 10010110.

What You Should See:

With the circuit complete, plug the Arduino in to a power source. Once powered, the buzzer will beep a few times, and all four LEDs should begin blinking. The game begins once you press any of the four buttons. Once the game has been started, a random LED will blink. Press the button associated with that color LED to replicate the pattern. With a successful guess, the pattern will repeat, this time adding another random LED. The player is to follow the pattern for as long as possible, with each successful guess resulting in an additional layer of complexity added to the original pattern.

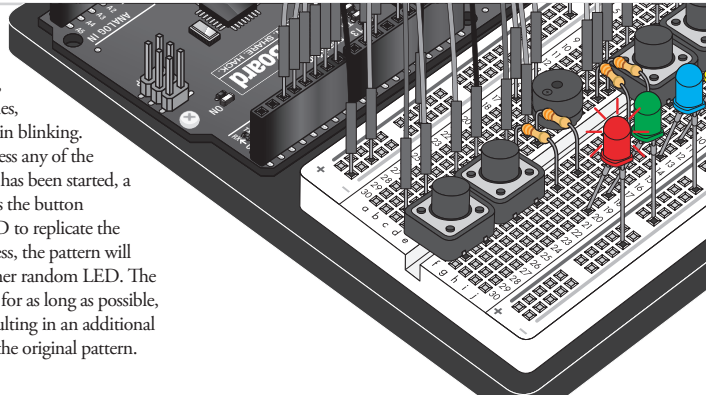

Troubleshooting:

Only half the circuit works

If only half of your circuit is working, make sure you added the additional wire from one ground rail to the other. Remember that breadboards have two power rails on each side and that these can be connected, or bussed, together to provide the power to both sides of the same circuit.

No sound

Once the buzzer is in the breadboard, it's hard to see the legs and which row they are connected to. If you aren't hearing any sound, make sure your wires are on the same row as the buzzer legs.

Game is not working

If everything starts up ok, but you're having trouble when it comes time to play the game, you may have a button or two misplaced. Pay close attention to which pin is connected to each button, as it matters which button is pressed when a particular color lights up.

Real World Application:

Toys and games, such as the original Simon from Milton Bradley, have relied on electronics to provide fun and entertainment to children across the world.

