

1.

**How is this circuit, or a circuit like it, used in everyday life? Provide at least three examples.**

---

---

---

---

---

## Did you get your LED turned on?

Great. Now you are going to add a dimmer switch to your LED on pin # 9.

=====

## 2.

**What user interface component will you need to use as a dimmer?**

---

---

---

### 3.

Add the necessary text to the `oneOnAtATime()` method for the code heavy way to add the dimmer.

## 4.

**There are three different way to add a dimmer without changing or adding code. Try to find one of these ways without destroying your LED.**

**5.**

**Draw a schematic of your circuit in the space to the right, adding your dimmer component so that it works. There are four different ways to do this.**

**6.**

**What other component does the dimmer component in this circuit act as?**

**7.**

The LED needs a PWM value that ranges from 0 – 255. The dimmer component gives you values from 0 – 1023. Write an equation below that will convert the value the dimmer component outputs to a LED friendly value.

---

**8.**

**The LED values 0 – 255 actually represent 256 different values. Why is that?**

---

---

---

**9.**

**Imagine your LED circuit (without dimmer) as a meter indicating a sensor reading. Decide what kind of sensor you would like to use as an input and describe in your own words what would cause the meter to rise and fall.**

---

## 5.

**Draw a logic flow chart of the LED with dimmer:**

[illegible]

## Circuit #4 Multiple LEDs

---