

Circuit #2 Potentiometers

1.

How is this circuit, or a circuit like it, used in everyday life? Provide at least three examples.

---

---

---

---

---

Can you turn your LED up and down using the potentiometer? Potentiometers are also called trimpots.

2.



Describe how the potentiometer is being adjusted according to the PWM diagram above.

---

---

---

---

---

---

---

---

3.

Who invented the potentiometer and when?

---

---

4.

What basic component does a potentiometer act like when it is not being adjusted?

---

---

5.

In your own words describe what voltage dividers do.

---

---

---

---

---

---

---

---

6.

Describe how you would use potentiometers to control a marshmallow (because they are soft) launcher's trajectory. What other pieces of hardware would you need to create this marsh-mallow launcher?

---

---

---

---

---

---

---

---

## Circuit #2 Potentiometers

---

Calculate percentage for each of the `analogWrite` values, then draw a line from the PWM code on the left to the corresponding PWM diagram on the right.

**7.**

`analogWrite (ledPin, 0);` \_\_\_\_\_ %

**8.**

`analogWrite (ledPin, 200);` \_\_\_\_\_ %

**9.**

`analogWrite (ledPin, 255);` \_\_\_\_\_ %

**10.**

`analogWrite (ledPin, 70);` \_\_\_\_\_ %

**11.**

`analogWrite (ledPin, 100);` \_\_\_\_\_ %

