

CIRCUIT #10

10

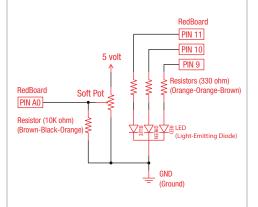


Soft Potentiometer

In this circuit, we are going to use yet another kind of variable resistor – this time, a soft potentiometer (or soft pot). This is a thin and flexible strip that can detect where pressure is being applied. By pressing down on various parts of the strip, you can vary the resistance from 100 to 10K ohms. You can use this ability to track movement on the soft pot, or simply as a button. In this circuit, we'll get the soft pot up and running to control an RGB LED.

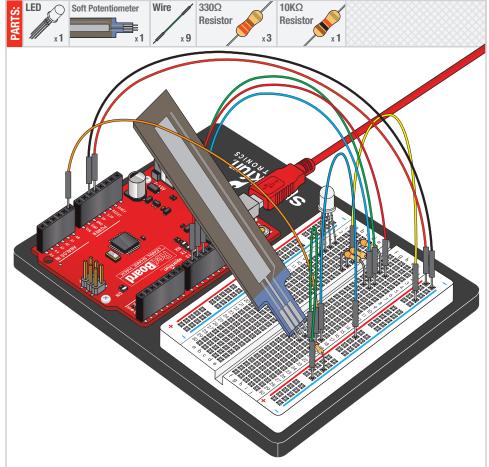

Page 57

Circuit 10: Soft Potentiometer

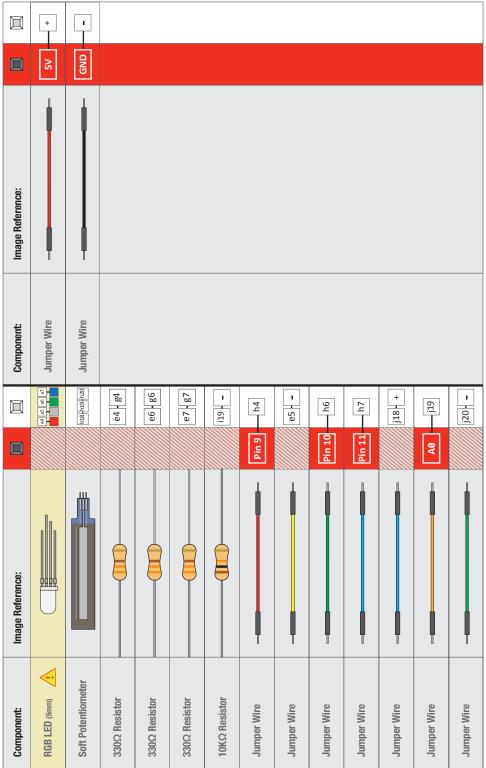

Page 59

10

Arduino Code:

Open Arduino IDE // File > Examples > SIK Guide > Circuit # 10

Code to Note:




redValue = constrain(map(RGBposition, 0, 341, 255, 0), 0, 255) + constrain(map(RGBposition, 682, 1023, 0, 255), 0, 255);

greenValue = constrain(map(RGBposition, 0, 341, 0, 255), 0, 255) - constrain(map(RGBposition, 341, 682, 0,255), 0, 255);

blueValue = constrain(map(RGBposition, 341, 682, 0, 255), 0, 255) - constrain(map(RGBposition, 682, 1023, 0, 255), 0, 255);

These big, scary functions take a single Value (RGBposition) and calculate the three RGB values necessary to create a rainbow of color. The functions create three "peaks" for the red, green, and blue values, which overlap to mix and create new colors. See the code for more information! Even if you're not 100% clear how it works, you can copy and paste this (or any) function into your own code and use it yourself. If you want to know more about creating your own functions - take a look at circuit #11.

What You Should See:

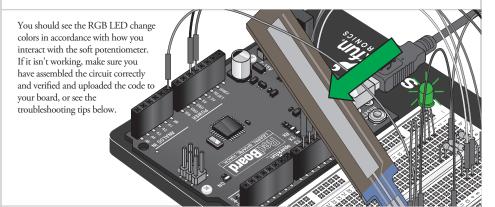

Troubleshooting:

LED Remains Dark or Shows Incorrect Color

With the four pins of the LED so close together, it's sometimes easy to misplace one. Try double checking each pin is where it should be.

Bizarre Results

The most likely cause of this is if you're pressing the potentiometer in more than one position. This is normal and can actually be used to create some neat results.

Real World Application:

The knobs found on many objects, like a radio for instance, are using similar concepts to the one you just completed for this circuit.

