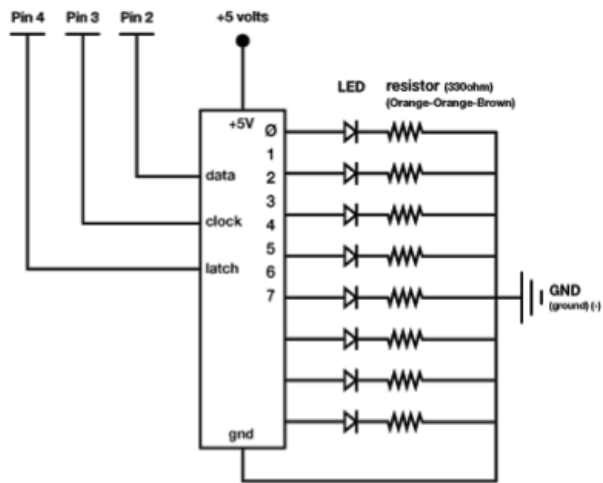


Circuit #14 Shift Register

Circuit:



A Little History:

6.

What was one of the first known uses of the shift register?

7.

This shift register and LED combination is a powerful display or interface circuit. Explain a sensor or two you might attach to this circuit and what the LEDs attached to the shift register would signify. Example: connect a mic and each LED would represent a different musical note heard by the mic.
